


Class:	CPE300L - Digital System Architecture and Design Lab			Semester:	Fall 2025
Points		Document author:	Darryll Mckoy		
		Author's email:	Mckoyd1@unlv.nevada.edu		
		Document topic:	Postlab 3		
Instructor's comments:					

1. Hours spent on this lab

About 10 hours (could not get the DE2 usb blaster to work)


2. Reaction timer black box diagram

Black Box Diagram:

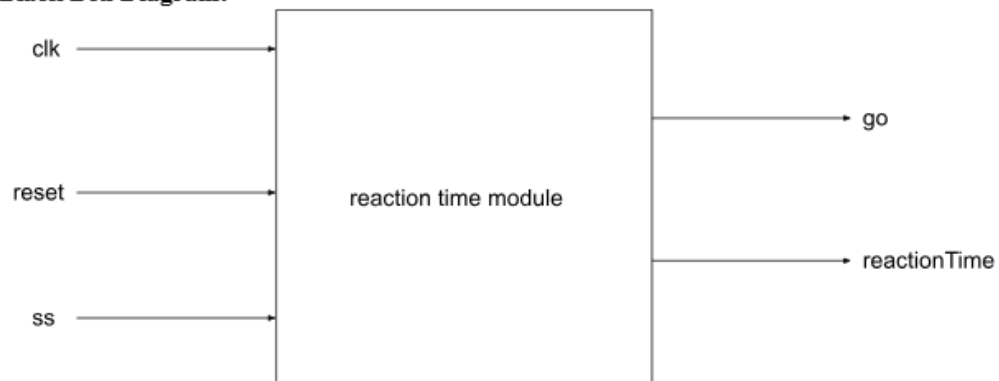

3. Reaction timer block diagram

Block Diagram:

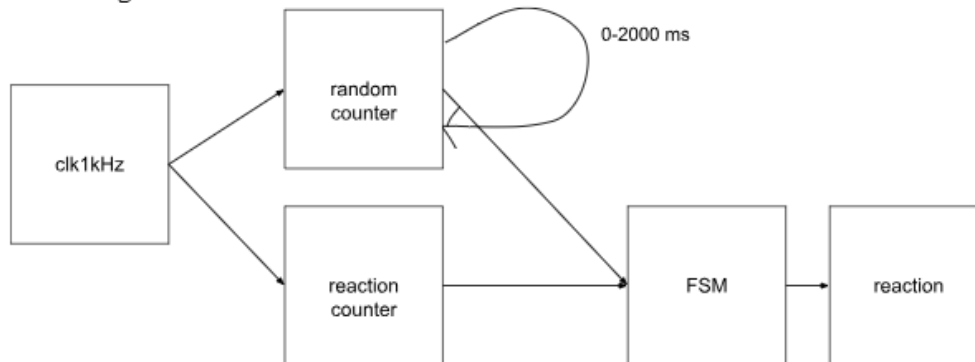

4. System Verilog code and submodules

Reaction sv code (reaction.sv)

```
1  //Structural system verilog reaction timer Code (Lab 3)
2  module reaction(    input logic clk, reset,
3                      input logic ss,
4                      output logic go,
5                      output logic [10:0] reactionTime
6  );
7
8      //internal signals
9      logic clk1k;
10     logic [31:0] msCnt;
11     logic [10:0] reactionCnt;
12     logic [10:0] rndmCnt;
13     logic capture;
14
15     //1 kHz clock submodule
16     clk1kHz u_div (
17         .clk(clk),
18         .reset(reset),
19         .clkout(clk1k)
20     );
21
22     //millisecond counter submodule
23     random_cnt u_reaction (
24         .random_clk(clk1k),
25         .reset(reset),
26         .cnt(reactionCnt)
27     );
```

```

28
29 //secondary counter for random time
30 random_cnt u_rand (
31     .random_clk(clk1k),
32     .reset(reset),
33     .cnt(rndmCnt)
34 );
35
36 //FSM submodule
37 reaction_FSM u_fsm (
38     .clk(clk1k),
39     .reset(reset),
40     .ss(ss),
41     .cnt(rndmCnt),
42     .go(go),
43     .capture(capture)
44 );
45
46 //reaction time register
47 always_ff @(posedge clk1k or posedge reset) begin
48     if (reset) begin
49         reactionTime <= 0;
50     end
51     else if (capture) reactionTime <= reactionCnt;
52 end
53
54 endmodule

```

1kHz clock sv code (clk1kHz.sv)

```

1
2 module clk1kHz(input logic clk, reset, output logic clkout);
3
4     logic [15:0] count = 0; // Counter to count clock cycles (e.g., 20 bits for 1M counts)
5     int value = 1000; // The number of clock cycles for 1 kHz
6     int clk_20kHz = 20000;
7
8     ///////////////////////////////////////////////////
9
10    // Frequency divider logic
11    always @(posedge clk or posedge reset) begin
12
13        if (reset) begin
14            count <= 16'd0;
15            clkout <= 1'b0;
16        end
17
18
19        else begin if (count == value) begin
20            count <= 16'd0;
21            clkout <= ~clkout;
22        end
23
24        else begin
25            count <= count + 1;
26        end
27    end
28
29 end
30 end
31
32 endmodule

```

Random counter sv code (random_cnt.sv)

```
1  /* random counter
2  This loops from 0 - 2000 */
3
4  module random_cnt(input  logic random_clk, reset,
5  output logic [10:0] cnt);
6
7      logic [10:0] rnd_count = 0;
8      int value = 10; // The number of clock cycles for 2000ms
9
10     //////////////////////////////////////
11     always @(posedge random_clk or posedge reset) begin
12
13         if (reset) begin
14             rnd_count <= 11'b0;
15             cnt <= 11'b0;
16         end
17
18
19         else begin if (rnd_count == value) begin
20             cnt <= 0;
21             rnd_count <= 11'b0;
22         end
23
24         else begin
25             rnd_count <= rnd_count + 1;
26             cnt <= rnd_count;
27         end
28     end
29
30
31 end
32
33 endmodule
34
```

Reaction FSM code (reaction_FSM.sv)

```
1  //CPE 300L, Lab3 reaction_FSM
2
3  module reaction_FSM(input logic clk, reset,
4      |               | input logic ss,
5      |               | input logic [10:0] cnt,
6      |               | output logic go, capture);
7
8
9      typedef enum logic [4:0] {S0, S1, S2, S3, S4} statetype;
10     statetype state, nextstate;
11
12     // state register
13     always_ff @(posedge clk, posedge reset) begin
14         if (reset) begin
15             state <= S0;
16             $display("reset pressed moving to state S0");
17         end
18
19         else begin
20
21             state <= nextstate;
22
23         end
24     end
25
26     // next state logic
27     always_comb begin
28
29         capture <= 1'b0;
30
31         case(state)
32
33             //////////S0 press ss to start system //////////
34             S0:    if (ss) begin
35                 |   //capture <= 1'b0;
36                 |   nextstate = S1;    //if ss pressed then move on to next state to start clock divider;
37                 |   $display("ss pressed moving to state S1");
38             end
39
40             else begin
41                 nextstate = S0;    //if ss not pressed then stay in current state.
42                 $display("ss not pressed staying in state S0");
43             end
44         end
```

```


45 ////////////// S1 start clock divider (50mhz to 1khz) in this state /////
46 S1: if (!ss) begin
47     nextstate = S2;
48     $display("initializing random counter");
49 end
50
51 else begin
52     nextstate = S1;
53     $display("waiting for clk divider to complete");
54 end
55
56 ////////////// S2 start random counter (loops from 0-2000) /////
57 S2: if (cnt == 1'd0) begin
58     nextstate = S3;
59     $display("cnt equal to 0 asserting go and moving to state S3");
60 end
61
62 else begin
63     nextstate = S2;
64     $display("waiting for cnt to reach zero!");
65 end
66
67 ////////////// S3 assert go (board LED gives signal) start reaction timer //////////
68
69 S3: if (ss) begin
70     nextstate = S4;
71     $display("starting reaction timer and moving to state S4");
72 end
73
74 else begin
75     nextstate = S3;
76     $display("ss not pressed staying in state S3");
77 end
78
79 ////////////// S4 capture reaction time, set go = 0, capture = 1 //////////
80
81 S4: if (!ss) begin
82     capture <= 1'b1;
83     //go <= ~go;
84     nextstate = S0;
85     $display("ss pressed asserting capture, outputting reaction time and moving to state S0");
86 end
87
88 else begin
89     nextstate = S4;
90     $display("ss not pressed staying in state S4");
91 end
92
93
94
95
96 default: begin
97     nextstate = S0;
98     //go = 1'b0;
99 end
100
101 endcase
102
103 end
104 // output logic
105 assign go = (state == S3);
106
107 endmodule

```


Reaction timer testbench (testbench_reaction.sv)

```
1  //reaction timer testbench (lab 3)
2
3  module testbench_reaction();
4      logic      clk, reset;
5      logic      ss, go;
6      logic [10:0] reactionTime;
7
8      // instantiate device under test
9      reaction dut(clk, reset, ss, go, reactionTime);
10
11     // generate clock
12     always
13     begin
14         clk = 1; #5; clk = 0; #5;
15     end
16
17     // at start of test, load vectors
18     // and pulse reset
19     initial
20     begin
21         reset = 1; #5; reset = 0;
22         ss = 1; #10;
23     end
24
25     endmodule
```

5. Reaction timer simulated waveform

 

 6. Screenshot of binary reaction time on DE2-115 board



Video demonstration: <https://youtu.be/7MMEMc39STY?si=XSUWIVGCfESqhqm5>

7. Feedback

Would recommend a video demonstration or screenshots of expected outcomes on DE2 board within the assignment instruction PDF.