 


Class:	CPE300L - Digital System Architecture and Design Lab	Semester:	Fall 2025
Points		Document author:	Darryll Mckoy
		Author's email:	Mckoyd1@unlv.nevada.edu
		Document topic:	Postlab 2
Instructor's comments:			

1. Hours spent on this lab

About 7 hours

2. FSM state transition diagram




3. FSM System Verilog code

```
C: > altera > 14.1 > FSM.sv
1 //CPE 300L, Lab2 FSM
2
3 module FSM(input logic clk, reset,
4           input logic ss,
5           input logic [31:0] cnt,
6           output logic go, capture);
7
8 typedef enum logic [1:0] {S0, S1, S2} statetype;
9 statetype state, nextstate;
10
11 // state register
12 always_ff @(posedge clk, posedge reset)
13   if (reset) begin
14     state <= S0;
15     $display("reset pressed moving to state S0");
16   end
17
18   else state <= nextstate;
19
20 // next state logic
21 always_comb
22   case (state)
23     S0: if (ss) begin
24         nextstate = S1; //if ss pressed then move on to next state and generate random value 0-3000;
25         $display("ss pressed moving to state S1");
26       end
27       else begin
28         nextstate = S0; //if ss not pressed then stay in current state.
29         $display("ss not pressed staying in state S0");
30       end
31
32     S1: if (cnt > 32'h0 && cnt < 32'hBB8) begin
33         nextstate = S2;
34         $display("cnt between 0-3000 asserting go and moving to state S2");
35       end
36       else begin
37         nextstate = S1;
38         $display("Error! cnt not between 0-3000 staying in S1");
39       end
40
41     S2: if (ss) begin
42         nextstate = S0;
43         $display("ss pressed asserting capture and moving to state S0");
44       end
45       else begin
46         nextstate = S2;
47         $display("ss not pressed staying in state S2");
48       end
49     default: nextstate = S0;
50   endcase
51
52 // output logic
53 assign capture = (state == S0);
54 assign go = (state == S2);
55 endmodule
```

FSM testbench code

```
C: > altera > 14.1 > testbench_FSM.sv
1  // 4.39: testbench example 3
2
3  module testbench_fsm();
4      logic      clk, reset;
5      logic      ss;
6      logic [31:0] cnt;
7      logic go, capture;
8
9      // instantiate device under test
10     FSM dut(clk, reset, ss, cnt, go, capture);
11
12     // generate clock
13     always
14     begin
15         clk = 1; #5; clk = 0; #5;
16         cnt = $urandom%5000; #10; |
17     end
18
19     // at start of test, load vectors
20     // and pulse reset
21     initial
22     begin
23         reset = 1; #10; reset = 0;
24         ss = 1; #10;
25
26         ss = 0; #10;
27         ss = 1; #10;
28     end
29
30 endmodule
```

4. FSM waveform

 


5. 1kHz clock system Verilog code

```
C: > altera > 14.1 > clk1kHz.sv
1
2 module clk1kHz(input logic clk, reset, output logic clkout);
3
4     logic [15:0] count = 0;    // Counter to count clock cycles (e.g., 20 bits for 1M counts)
5     int value = 1000; // The number of clock cycles for 1 kHz
6     int clk_20kHz = 20000;
7
8     //////////////////////////////////////
9
10    // Frequency divider logic
11    always @(posedge clk or posedge reset) begin
12
13        if (reset) begin
14            count <= 16'd0;
15            clkout <= 1'b0;
16        end
17
18
19        if (count == value) begin
20            count <= 16'd0;
21            clkout <= ~clkout;
22        end
23
24        else begin
25            count <= count + 1;
26        end
27    end
28
29 end
30
31
32 endmodule
```

1kHz clock testbench code

```
C: > altera > 14.1 > clk1kHz_testbench.sv
1  //1kHz testbench
2
3  module testbench_clk1kHz();
4      logic      clk, reset;
5      logic      clkout;
6
7
8      // instantiate device under test
9      clk1kHz dut(clk, reset, clkout);
10
11
12     // generate clock
13     always
14     begin
15         clk = 1; #5 clk = 0;
16     end
17
18
19     initial
20     begin
21         reset = 1; #5 reset = 0;
22     end
23
24     //toggle clock at positive clock edge
25     always @(posedge clk)
26     begin
27         //reset = 1; #5 reset = 0;
28         clk = 1; #5; clk = 0; #5;
29     end
30
31
32 endmodule
```

6. 1kHz clock waveform

 


7. Millisecond counter system Verilog code

```
C: > altera > 14.1 > ≡ mscnt.sv
1  module mscnt(input  logic clk, reset,
2  output logic [31:0] cnt);
3
4
5  logic [15:0] count = 0;  // Counter to count clock cycles
6  int value = 1000; // The number of clock cycles for 1 kHz
7  int clk_20kHz = 20000;
8
9  //////////////////////////////////////////
10
11
12  always @(posedge clk or posedge reset) begin
13
14      if (reset) begin
15          count <= 16'd0;
16          //clkout <= 1'b0;
17          cnt <= 32'b0;
18      end
19
20
21      if (count == value) begin
22          count <= 16'd0;
23          //clkout <= ~clkout;
24          cnt <= cnt + 1;
25      end
26
27      else begin
28          count <= count + 1;
29      end
30  end
31
32  end
33
34
35  endmodule
```


Millisecond counter system Verilog testbench code

```
C: > altera > 14.1 > mscnt_testbench.sv
1  //millisecond counter testbench
2
3  module testbench_mscnt();
4      logic      clk, reset;
5      logic      [31:0] cnt;
6
7
8      // instantiate device under test
9      mscnt dut(clk, reset, cnt);
10
11
12     // generate clock
13     always
14     begin
15         |   clk = 1; #5 clk = 0;
16     end
17
18
19     initial
20     begin
21         |   reset = 1; #5 reset = 0;
22     end
23
24     //toggle clock at positive clock edge
25     always @(posedge clk)
26     begin
27         //reset = 1; #5 reset = 0;
28         clk = 1; #5; clk = 0; #5;
29
30     end
31
32 endmodule
```

8. Millisecond counter waveform

 

9. Feedback

No complaints.